



POLITECNICO
MILANO 1863

Phase-Locked Loop (PLL)

basic concepts

AA 2020-2021

Prof. William Fornaciari


Politecnico di Milano

Dip. di Elettronica, Informazione e Bioingegneria

william.fornaciari@polimi.it



 - A **phase-locked loop (PLL)** is an electronic circuit that consists of a phase detector, a low-pass filter, and a voltage-controlled oscillator (VCO) connected in a loop
- The closed-loop operation of the circuit is to **maintain the VCO frequency locked to that of the input signal frequency**





- **Frequency synthesizers that provide multiples of a reference signal frequency**
- FM demodulation networks for FM operation with excellent linearity between the input signal frequency and the PLL output voltage
- Demodulation of the two data transmission or carrier frequencies in digital-data transmission used in frequency-shift keying (FSK) operation.
- Wide variety of areas including modems, telemetry receivers and transmitters, tone decoders, AM detectors, and tracking filters, embedded systems, computing




■ Capture and Lock operation

- Within a capture-and-lock frequency range, the dc voltage will drive the VCO frequency to match that of the input
- While the loop is trying to achieve lock, the output of the phase comparator contains frequency components at the sum and difference of the signals compared
- A low-pass filter passes only the lower frequency component of the signal, so that the loop can obtain lock between input and VCO signals




■ Lock operation

- Input signal frequency is the same as that from the VCO
- Best operation is obtained if the VCO center frequency f_0 is set with the dc bias voltage midway in its linear operating range
- The amplifier allows this adjustment in dc voltage from that obtained as output of the filter circuit
- When the loop is in lock, the two signals to the comparator are of the same frequency, although not necessarily in phase
- A fixed phase difference between the two signals to the comparator results in a fixed dc voltage to the VCO
- Changes in the input signal frequency then result in change in the dc voltage to the VCO

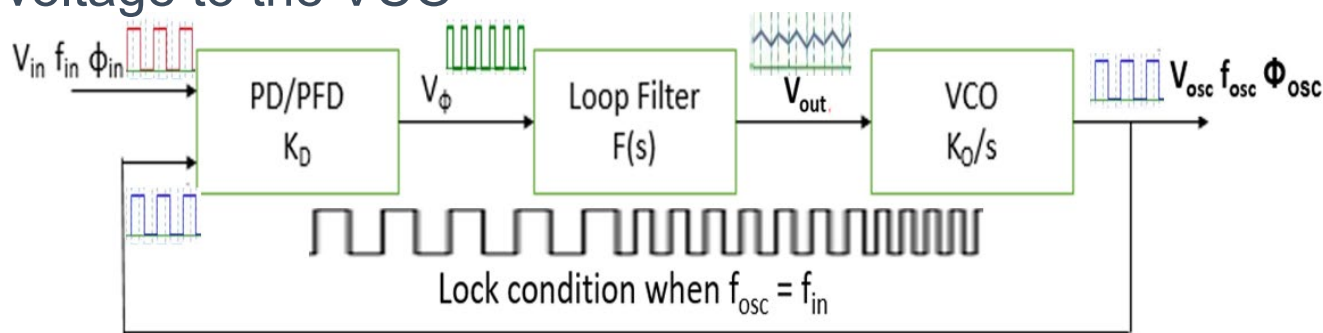



- Owing to the limited operating range of the VCO and the feedback connection of the PLL circuit, there are **two** important **frequency** bands specified for a PLL
- The **capture** range of a PLL is the frequency range centered about the VCO free-running frequency f_0 over which the loop can acquire lock with the input signal
- Once the PLL has achieved capture, it can maintain **lock** with the input signal over a somewhat wider frequency range called the lock range

 





- **Clock multiplier/Clock Generator**
 - Input: Fixed frequency clock
 - Output: Multiple of input clock frequency/Multiple of clock outputs
- **Frequency synthesizer (Fractional-N, Integer-N)**
 - Input: Fixed frequency clock
 - Output: Clock signal with arbitrary frequency
- **Clock and data recovery**
 - Input: Data signal (from a serial link)
 - Output: Digital data as well as clock signal with phase detector is different than other applications
- **FM demodulation**
 - Input: Radio signal
 - Output: Demodulated signal



 - A frequency **divider** is inserted between the VCO output and the phase comparator so that the loop signal to the comparator is at frequency f_o and the VCO output is **Nf_o**
- This output is a **multiple** of the input frequency as long as the loop is in lock




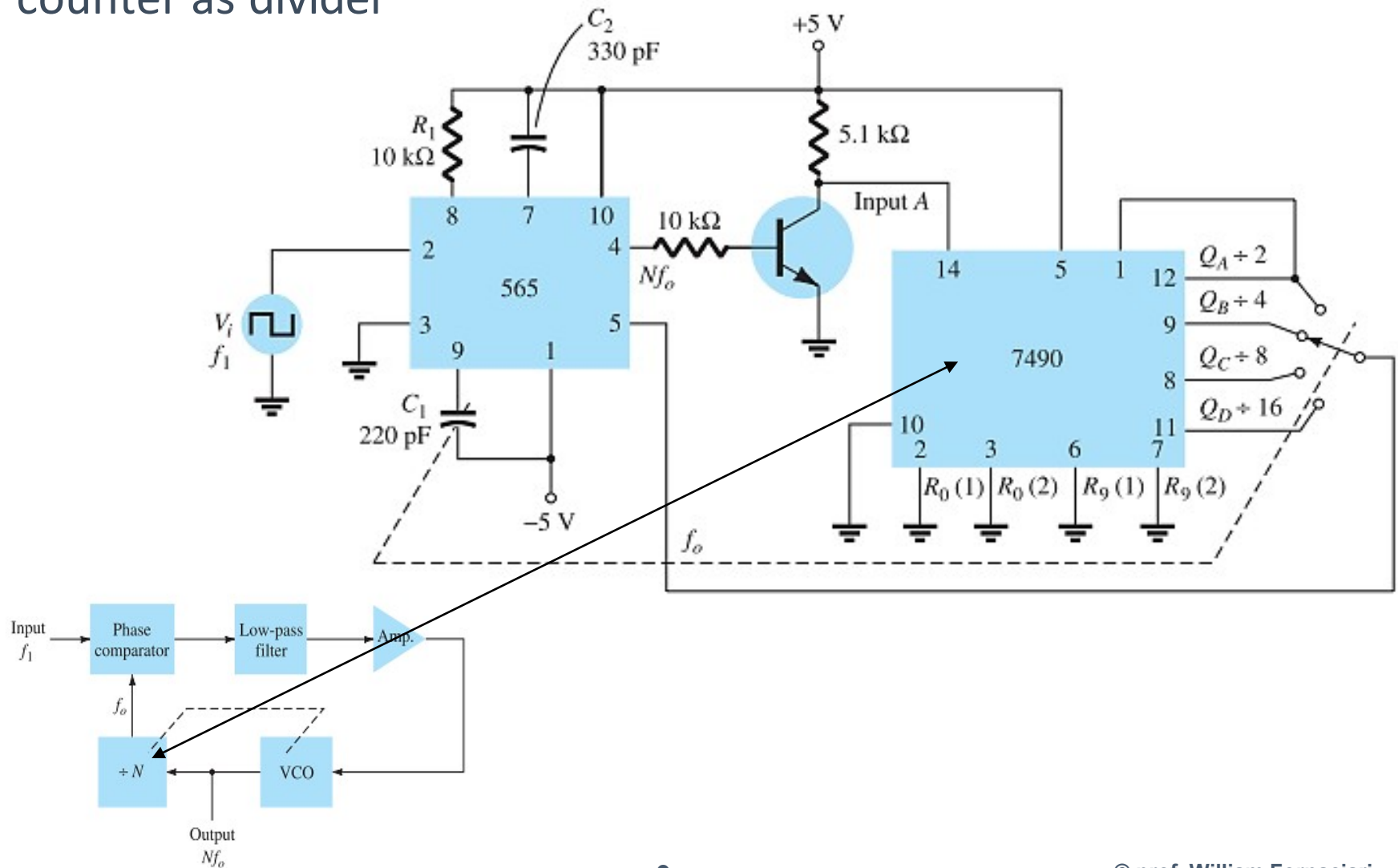- Example using a 565 PLL as frequency multiplier and a 7490 counter as divider





- The resolution of the output frequency is determined by the reference frequency applied to the phase detector
 - Step size or frequency resolution - the smallest frequency increment possible
- To obtain a stable low frequency source is not easy, because a quartz crystal oscillating in kHz region is quite bulky and not practical
 - A sensible approach is to take a good stable crystal-based high frequency source and an integer-N synthesizer to divide it down

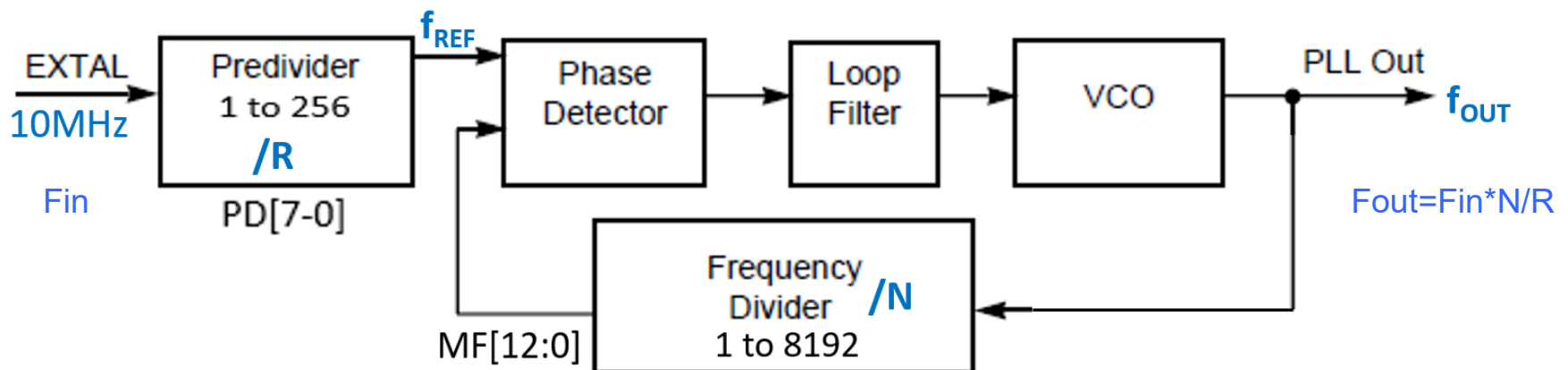



Programmable Phase-Locked Loop Clock Generator

- The FS7140/FS7145 is a monolithic CMOS clock generator/regenerator IC. Via the I2C-bus interface, the FS7140/45 can be adapted to many clock generation requirements. The length of the reference and feedback dividers, their fine granularity and the flexibility of the post divider make the FS7140/45 a very flexible stand alone PLL clock generator

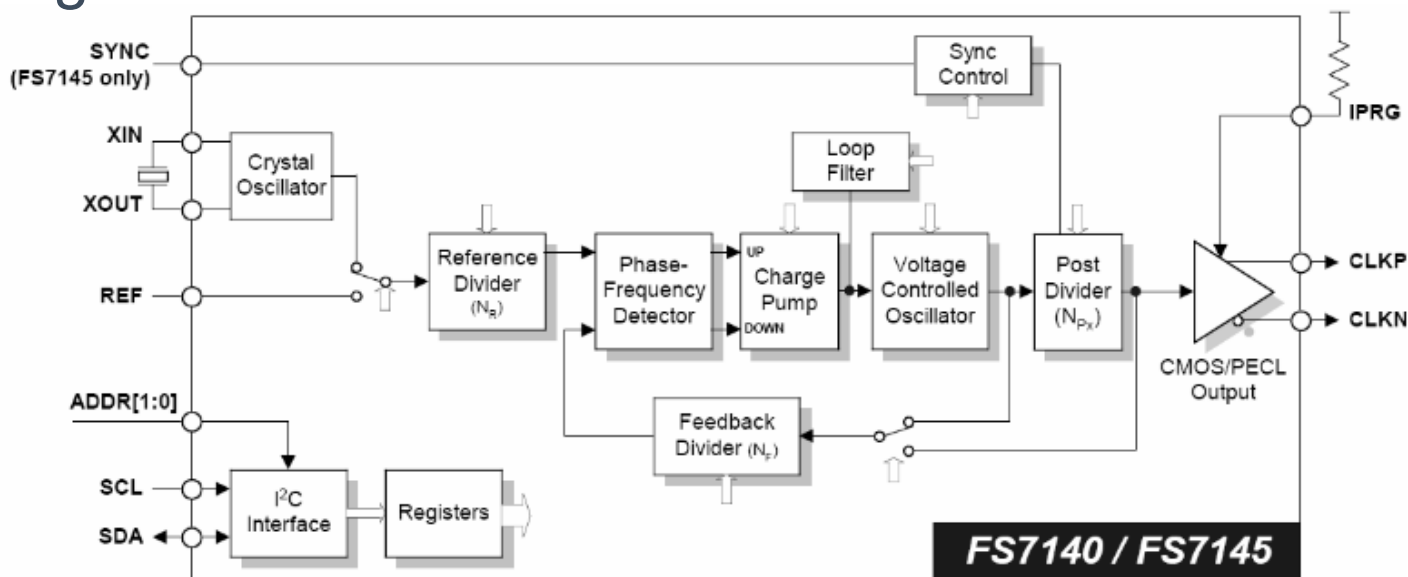


Figure 1. Device Block Diagram



What to remember for our purposes

- PLLs allows to generate a new frequency with a formula like $F_{out} = F_{ref} \cdot (N/R)$
 - N and R can be selected by the ES designer, not all of them are valid, there are some steps and constraints
- The stability of the referece freq. can be that of a XTAL
- Multiple frequencies can be obtained from the same XTAL in a programmable way
 - Creation of clock domains
 - Variable speed based on variable computing needs
- Use of prescalers
 - To extend the upper frequency range of a frequency synthesizer but still allowing the synthesis of lower frequencies
- In MCUs usually the clock frequency is fixed at design time
- High-end embedded systems tends to allow modifying dynamically the frequency to save power and for thermal



Integer-N Frequency Synthesizers with Prescalers

■ Four-modulus prescalers

- To extend the upper frequency range of a frequency synthesizer but still allows the synthesis of lower frequencies. The solution is the four-modulus prescaler
- The four-modulus prescaler is a logical extension of the dual-modulus prescaler. It offers four different scaling factors, and two control signals are required to select one of the four available scaling factors

